

Homework #1 (7장)

7.1.1 전류가 $i(t) = 10 \cos(314t - 60^\circ)$ A일 때, 전류의 주기와 헤르츠 단위의 주파수를 계산하라.

풀이:

$$\begin{aligned} W &= 314 = 2\pi f \\ \rightarrow 2\pi f &= 314 \\ \Leftrightarrow f &= \frac{314}{2\pi} [Hz] \\ \rightarrow T &= \frac{1}{f} = \frac{2\pi}{314} \end{aligned} \quad \therefore T = \frac{2\pi}{314}, f = \frac{314}{2\pi} [Hz]$$

7.1.3 다음의 전압과 전류가 주어질 때,

$$i(t) = 5 \sin(314t + 30^\circ) \text{ V}$$

$$v(t) = 10 \cos(314t - 20^\circ) \text{ V}$$

$i(t)$ 와 $v(t)$ 간의 위상 관계를 구하라.

풀이:

$$i(t) = 5 \sin(314t + 30^\circ)$$

$$= 5 \cos(314t + 30^\circ - 90^\circ)$$

$$= 5 \cos(314t - 60^\circ)$$

$$\rightarrow \theta_i = -60^\circ$$

$$V(t)'s \theta_v = -20^\circ$$

$$\rightarrow \theta_i - \theta_v = -60^\circ - (-20^\circ) = -40^\circ$$

$\therefore i(t)$ 는 $v(t)$ 보다 40° 앞.

$= |i(t)|$ 와 $v(t)$ 의 $t=0$ 일 때.


$= |i(t)|$ 와 $v(t)$ 의 $t=0$ 일 때.

7.4.2 그림 P7.4.2에서 아래의 전압이 인가되었을 때 커패시터에 흐르는 전류를 계산하라.

(a) $v_1(t) = 20 \cos(314t - 60^\circ) \text{ V} = 20 \angle -60^\circ$ $W: 314$

(b) $v_2(t) = 24 \sin(314t + 30^\circ) \text{ V} = 24 \angle 30^\circ$ $W: 314$

해답은 주파수 및 시간 영역에서 모두 표현하라.

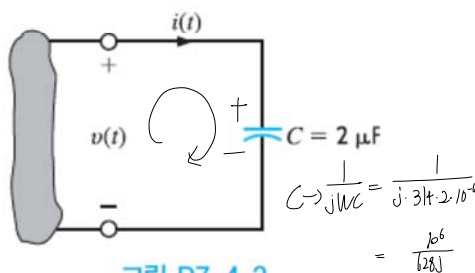

풀이:

(a)

$$20 \angle -60^\circ = \frac{10^6}{628j} \cdot i$$



$$\rightarrow i = \frac{20 \angle -60^\circ}{\frac{10^6}{628j}} \cdot 628j$$

$$= \frac{10 \angle -60^\circ}{10^5} \cdot 628j$$

$$= \frac{1 \angle -60^\circ}{10^4} \cdot 628j$$

$$= (j + \sqrt{3}) \cdot \frac{628}{10^4}$$

$$= (j + \sqrt{3}) 62.8 \text{ mA} \quad (\cos > \sin)$$

$$\rightarrow 2 \times 62.8 = 125.6$$

$$\therefore \text{결과: } (j + \sqrt{3}) 62.8 \text{ mA} \quad (\cos > \sin)$$

$$\text{또는 } 125.6 \cos(314t + 60^\circ) \text{ mA} \quad (\cos > \sin)$$



(b) $24 \angle 30^\circ = \frac{10^6}{628j} \cdot i$

$$\rightarrow i = \frac{24 \angle 30^\circ}{\frac{10^6}{628j}} \cdot 628j$$

$$= \frac{12 \angle 30^\circ}{10^5} \cdot 628j$$

$$= 62.8 \angle (30^\circ - 90^\circ) \text{ mA}$$
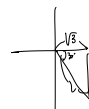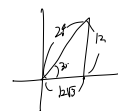
$$= 75.36 \angle (-60^\circ) \text{ mA} \quad (\sin > \cos)$$




$$\rightarrow 2 \times 75.36 = 150.72$$

$$\therefore \text{결과: } 75.36 \angle (-60^\circ) \text{ mA} \quad (\sin > \cos)$$


$$\text{또는 } 150.72 \sin(314t - 30^\circ) \text{ mA} \quad (\sin > \cos)$$

$$f = 50 \rightarrow \omega = 2\pi f = 100\pi$$

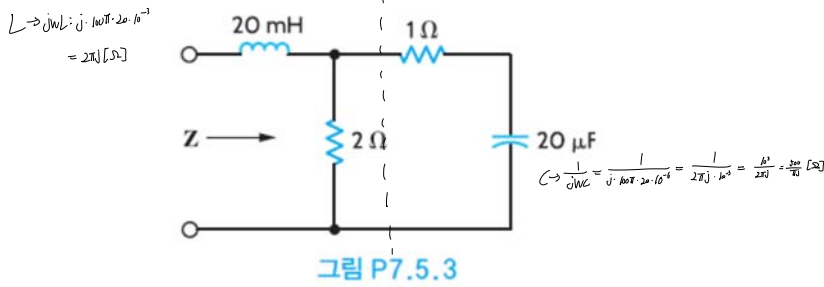7.5.3 그림 P7.5.3 회로망에서 주파수가 50 Hz일 때, 주파수 영역 임피던스 Z 를 구하라.



풀이:

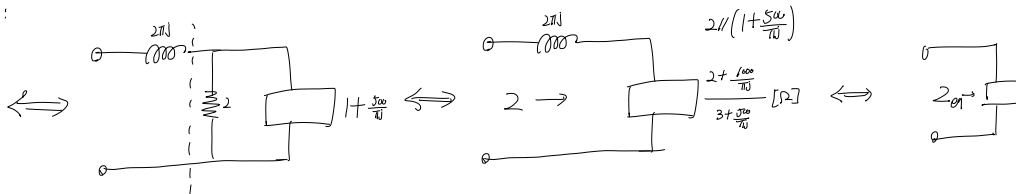

$$2 \parallel \left(1 + \frac{j1000}{2\pi}\right) = \frac{2 \cdot \left(1 + \frac{j1000}{2\pi}\right)}{2 + \left(1 + \frac{j1000}{2\pi}\right)} = \frac{2 + \frac{j1000}{\pi}}{3 + \frac{j1000}{2\pi}} [\Omega]$$

$$Z_{eq} = 2\pi j + \frac{2 + \frac{j1000}{\pi}}{3 + \frac{j1000}{2\pi}} [\Omega]$$


$$= 2\pi j + \frac{2\pi j + 1000}{2\pi j + 3\pi} [\Omega]$$

$$= \frac{2\pi j(2\pi j + 3\pi) + 1000}{2\pi j + 3\pi} [\Omega]$$

$$= \frac{-6\pi^2 + j12\pi^2 + 1000}{2\pi j + 3\pi} [\Omega]$$

$$\therefore Z_{eq} = \frac{-6\pi^2 + j12\pi^2 + 1000}{2\pi j + 3\pi} [\Omega]$$

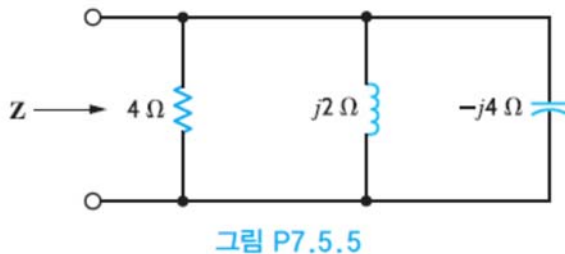7.5.5 그림 P7.5.5 회로망에서 주파수 영역 임피던스 Z 를 구하라.



풀이: $R \rightarrow R: 4\Omega$
 $L \rightarrow j\omega L: 2j\Omega$
 $C \rightarrow \frac{1}{j\omega C}: -4j\Omega$

$$\rightarrow Z_{eq} = 4 \parallel 2j \parallel -4j = \frac{1}{\frac{1}{4} + \frac{1}{2j} + \frac{1}{-4j}}$$

$$\rightarrow \frac{1}{\frac{1}{4} + -\frac{j}{2} + \frac{j}{4}}$$

$$= \frac{\frac{1}{1 - 2j + j}}{\frac{1}{4}} = \frac{4}{1 - j} \times \frac{1 + j}{1 + j} = \frac{4(1 + j)}{1 + 1} = 2 + 2j$$

$$\therefore Z_{eq} = 2 + 2j [\Omega]$$

7.6.2 그림 P7.6.2에서 $i_s(t)$ 가 $1 \cos(2500t - 45^\circ)$ A일 때 주파수 영역 회로를 그리고 $v_o(t)$ 를 계산하라. 또한, 패이지도를 이용하여 $i_C(t) + i_R(t) = i_s(t)$ 임을 보여라.

풀이:

$$\cos(2500t - 45^\circ) = i_s(t)$$

$$= 1 \angle -45^\circ \quad \omega = 2500$$

$$= \frac{1}{\sqrt{2}} - \frac{j}{\sqrt{2}}$$


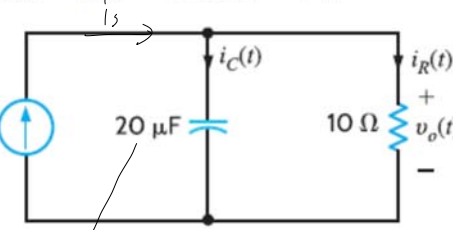


그림 P7.6.2

$$C \rightarrow \frac{1}{j\omega C} = \frac{1}{j \cdot 2500 \cdot 20 \cdot 10^{-6}} = \frac{1}{50j \cdot 10^{-3}} = \frac{10^3}{50j} = \frac{20}{j} = -20j \quad [\Omega]$$

$$R \rightarrow R = 10 \Omega$$

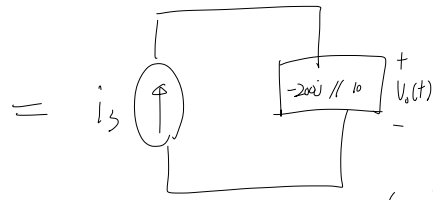


$$\rightarrow Z_{eq} = -20j // 10 = \frac{(-20j) \cdot 10}{-20j + 10} = \frac{-20j}{1 - 2j} \cdot \frac{(1 + 2j)}{(1 + 2j)} = \frac{-20j + 40}{5} = -4j + 8$$

$$KVL \rightarrow V_o(t) = i_s \cdot (8 - 4j) = \frac{1}{\sqrt{2}} (1 - j) (8 - 4j) = \frac{1}{\sqrt{2}} (8 - 4j - 4j - 4) = \frac{1}{\sqrt{2}} (4 - 8j) = 4\sqrt{2} \angle -71.57^\circ [V]$$

$$\rightarrow i_C(t) = \frac{V_o(t)}{-20j} = \frac{4\sqrt{2} \angle -71.57^\circ}{20 \angle -90^\circ} = \frac{\sqrt{2}}{5} \angle 18.43^\circ [A]$$

$$\rightarrow i_R(t) = \frac{V_o(t)}{10} = \frac{4\sqrt{2} \angle -71.57^\circ}{10 \angle 0^\circ} = \frac{2\sqrt{2}}{5} \angle -71.57^\circ [A]$$
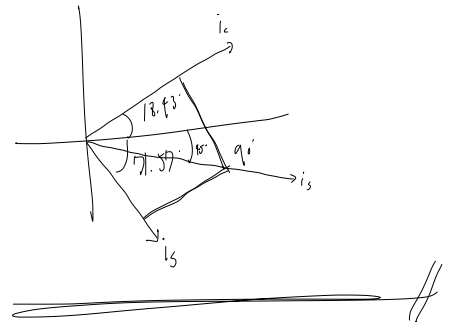
$$\therefore V_o = 4\sqrt{2} \angle -71.57^\circ [V]$$



7.7.4 그림 7.7.4에서 주파수 영역 전압 V_o 를 구하라.


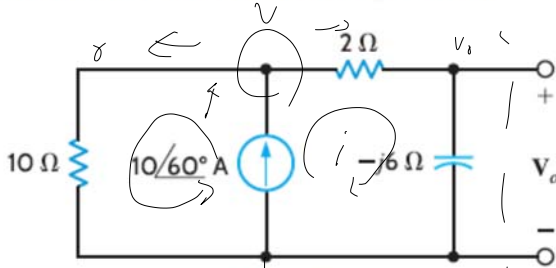


그림 P7.7.4

풀이:

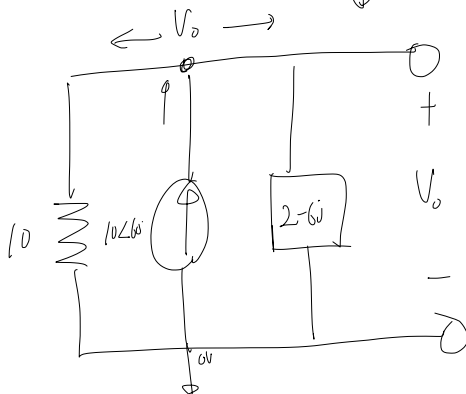

$$10 \angle 60^\circ = \frac{V_o - 0}{10} + \frac{V_o - 0}{2 - 6j}$$

$$= \frac{V_o}{10} + \frac{V_o(1 + 3j)}{20}$$

$$5 + 5\sqrt{3}j = \frac{V_o(2 + 3j)}{20}$$

$$V_o = \frac{20}{2 + 3j} \cdot 5(1 + \sqrt{3}j)$$

$$= \frac{100}{5} (1 + \sqrt{3}j)(1 - j) \cdot \frac{1}{2}$$

$$= \frac{20}{5} (1 - j + \sqrt{3} + \sqrt{3}j)$$

$$= \frac{20}{5} [1 + \sqrt{3} + j(\sqrt{3} - 1)]$$

$$\therefore \frac{50}{3} [1 + \sqrt{3} + j(\sqrt{3} - 1)] [V]$$

7.7.8 그림 7.7.8 회로에서 주파수 영역 전류 I 를 구하라.


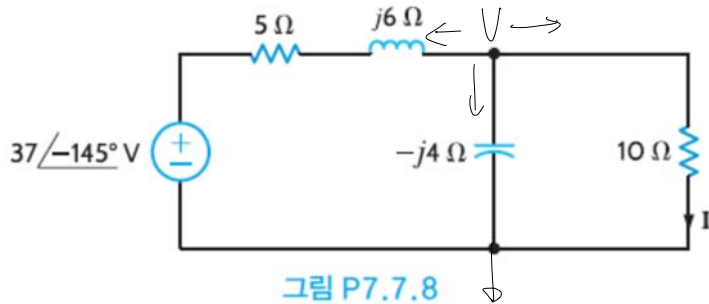


그림 P7.7.8

풀이:

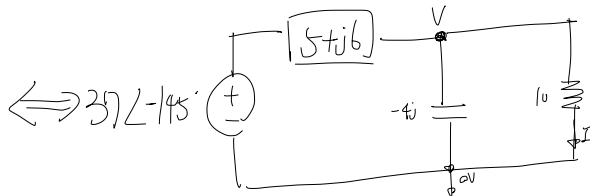

$$\rightarrow \frac{V - (37\angle -145^\circ)}{5+j6} + \frac{V}{-j4} + \frac{V}{10} = 0$$

$$\rightarrow V = 22\angle 25^\circ = -11.472 + j16.383 \text{ V}$$

$$\rightarrow I = \frac{V}{10} = \frac{-11.472 + j16.383}{10} = -1.1472 + j1.6383 \text{ A}$$

$$\therefore I = -1.1472 + j1.6383 \text{ A}$$

7.8.3 그림 7.8.3 회로에서 노드 해석을 이용하여 전압 V_o 를 구하라.


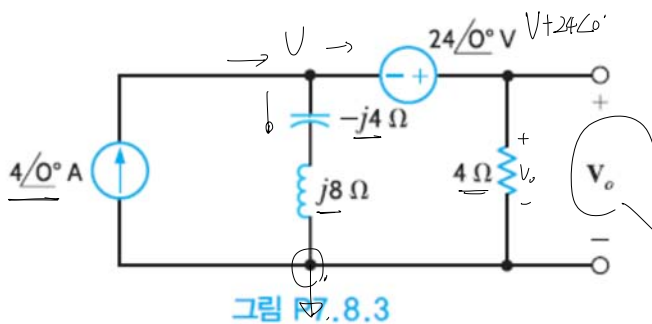



그림 7.8.3

풀이:

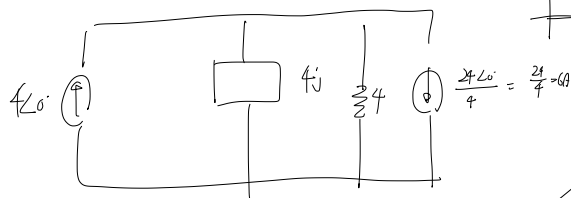


$$\therefore V_o = -4(1-j) \text{ V}$$

정답 2.66%

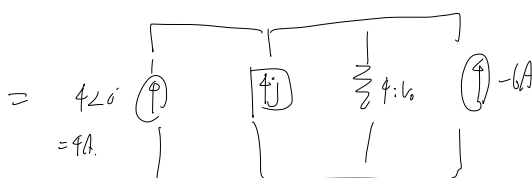

$$= -2A$$

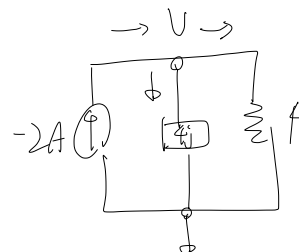


$$\therefore -2 = \frac{V_o}{4} + \frac{V}{4}$$

$$\Leftrightarrow -2 = \frac{V_o}{4} + \frac{V}{4}$$

$$-8 = V(1-j)$$

$$V = \frac{-8}{1-j} \cdot \frac{1+j}{1+j} = \frac{-8(1+j)}{2} = -4(1+j)$$

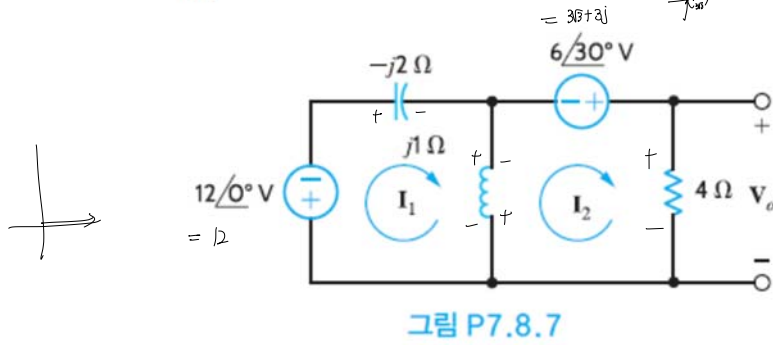7.8.7 그림 7.8.7 회로에서 망로 해석을 이용하여 전압 V_o 를 구하라.



풀이:

KVL at Mesh 1: $12 = -j2I_1 + j1(I_1 - I_2)$
 $12 = -jI_1 - jI_2$

KVL at Mesh 2: $3\sqrt{3} + j = j(I_2 - I_1) + 4I_2$
 $3\sqrt{3} + j = -jI_1 + (4+j)I_2$


→ $12 = -jI_1 - jI_2$
 $-j(3\sqrt{3} + j) = -jI_1 + (4+j)I_2$
 $12 - 3\sqrt{3} - j = (-j-2)I_2$

→ $I_2 = \frac{(12 - 3\sqrt{3} - j)}{(-j-2)}$
 $= \frac{(6\sqrt{3} - 12 + j)}{4 + j}$

→ $V_o = 4I_2 = 4 \cdot \frac{(6\sqrt{3} - 12 + j)}{4 + j}$
 $= \frac{2(6\sqrt{3} - 12 + j)}{2 + j} (2 - j)$
 $= \frac{2}{4 + j} (10 - 30j - 24 + 24j + 2 + j)$
 $= \frac{2}{4 + j} (18 - 6j + j)$
 $= \frac{2}{4 + j} (18 - 5j)$


∴ $V_o = \frac{2}{4 + j} (18 - 5j)$ (V)

7.8.9 문제 7.8.3을 중첩의 원리를 이용하여 구하라.

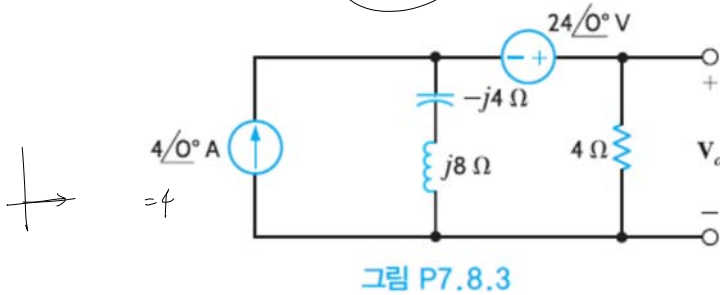


풀이:

1) 전압원 제거 → 단락 (= 0V)

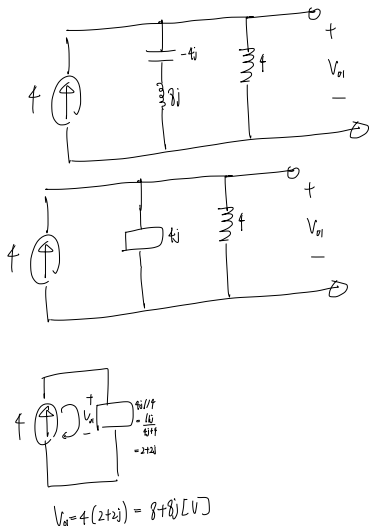


2) 전류원 제거 → 개방 (i = 0A)

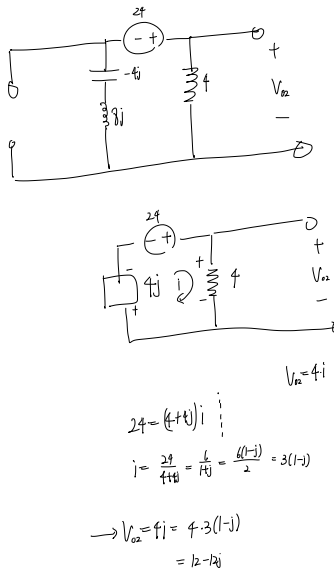






$V_o = V_{o1} + V_{o2}$
 $= (8+j) + (4-4j)$
 $= 12-3j$

∴ $V_o = 12-3j$ (V)

7.8.11 문제 7.8.3을 테브난의 정리를 이용하여 구하라.

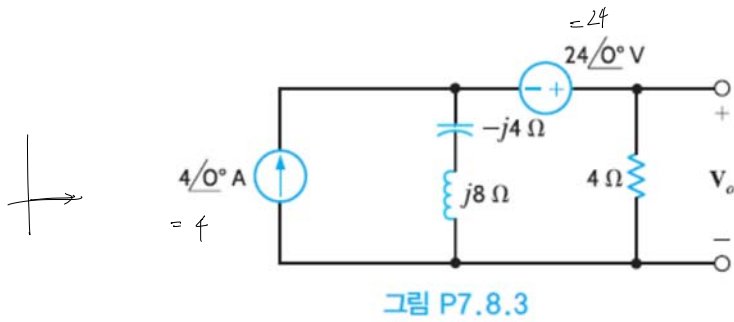

테이:

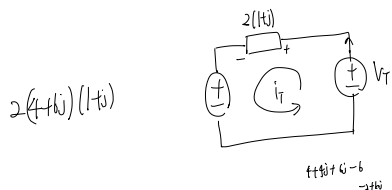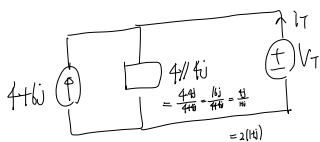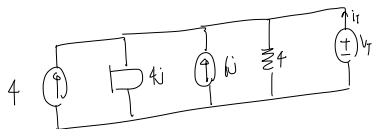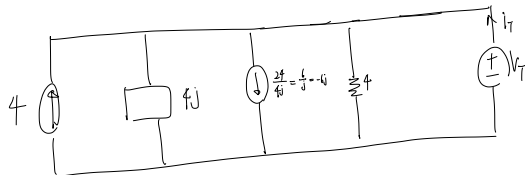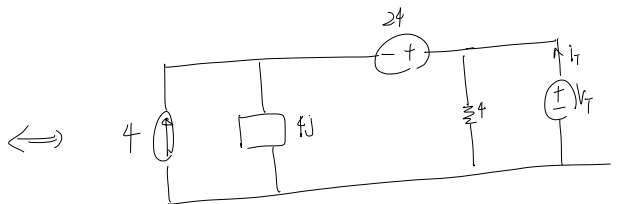

$$V_T = [2(4+j)] i_T + 2(4+j)(1+j)$$

$$V_T = (2+j2) i_T + (-4+2j)$$

$$\rightarrow 11j - 2 + 2j$$

$$V_{oc} = -4 + 2j$$

$$\therefore V_o = -4 + 2j \text{ [V]}$$